



**Trinity  
College  
Dublin**

The University of Dublin

**CS2022 Computer Architecture**

**Michael Manzke**

**Project 2**

**MICROCODED INSTRUCTION SET PROCESSOR**


**Student Name:** Alexandra Silva

**Student Number:** 15325158

## Table of contents


• Register	Page 3
• Mux2_1	Page 3
• Mux2_8	Page 3
• Mux2_16	Page 4
• Mux3_1	Page 4
• Mux8_1	Page 4
• Mux9_16	Page 5
• Decoder	Page 5
• Full Adder	Page 5
• Ripple Adder	Page 6
• Shifter	Page 6
• Circuit B	Page 6
• Circuit A to B	Page 7
• Instruction	Page 7
• Zero Fill	Page 7
• Program Counter	Page 7
• Extend	Page 8
• Arithmetic Logic Unit	Page 8
• Function Unit	Page 8
• Control Address Register	Page 8
• Memory	Page 9
• Control Memory	Page 9
• Register File	Page 9
• Datapath	Page 10
• Microprogrammed Control	Page 10
• Full Microprocessor	Page 10

## Register

 


The register is basically the same code used in the previous assignments. It works as expected for each edge when the signal is high on a given rising clock.

## Mux2\_1

 


In this multiplexer the values change between 0 and 1 and the output changes accordingly.

## Mux2\_8

 


This multiplexer takes the various inputs and produces an 8 bit output.

## Mux2\_16

 


This multiplexer goes through a series of changes as S goes between the values of 1 and 0. The output switches between the values of in0 and in1.

## Mux3\_1

 


This multiplexers output, Z, changes values according to the changing inputs of in0, in1, in2, s0 and s1.

## Mux8\_1

 

This multiplexer takes in various inputs and produces a 1 bit output.

## Mux9\_16

 


This multiplexer cycles through in0 to in 8 and takes all combinations of its inputs s0 to s3 to get the output signal Z.

## Decoder




This waveform is correct as it goes through every possible combination of inputs, causing each and every output to turn high via register selection.

## Full Adder

 

The full adder determines the correct carry for each input. Then the appropriate operations are performed resulting in the output shown.

## Ripple Adder

 


The ripple adder has two inputs of 16 bits A and B. It determines the Cin, Cout and Vout flags which will all be either 0 or 1. The output Gout then gathers all this information to produce the signal shown.

## Shifter




The shifter outputs left and right shifts according to the inputs given by B and S.

## Circuit B

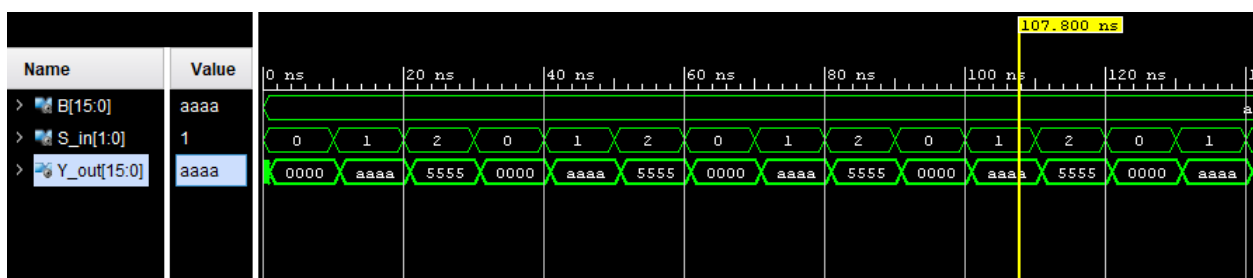


Logic Circuit B provides an output depending on the constant input B and the varying input Sin.

## Circuit A to B

 


Logic Circuit A to B has a selection pin that determines the operations that will be performed on the inputs. This is what causes the output to change despite the two constant inputs.

## Instruction

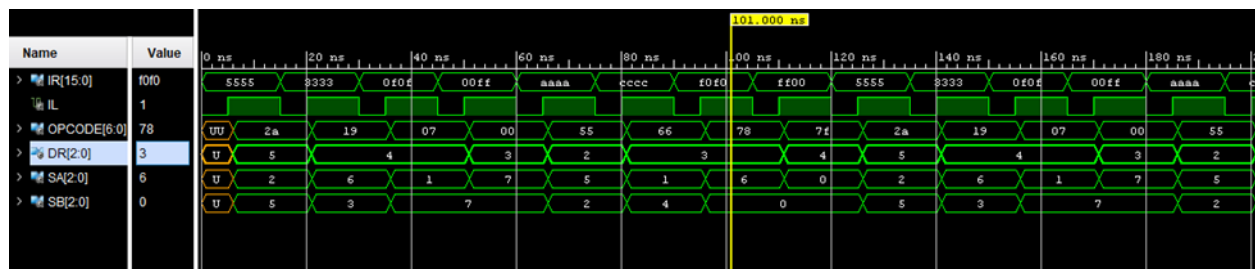


Instruction has 4 outputs and 3 inputs. The way it works is that it loads an instruction from memory and performs it on the inputs. This then gives us our outputs.

## Zero Fill

 


Zero Fill simply changes the input SB. As seen the output correlates to the changing input.


## Program Counter

 

## Extend

 


## Arithmetic Logic Unit

 


This gives us the output G using the given inputs and a select

## Function unit

 

This raises the N, Z, C and V flags

## Control Address Register

 



This shows the registers, decoder and multiplexer8\_16 working together. There is a slight delay at the beginning due to the amount of entities working and initializing. Output B is undefined for about 10ns



